

## APPENDIX L

# ANSWERS TO SELECTED PROBLEMS

### Chapter 1

- 1.1** (a)  $I = 0.5 \text{ mA}$ ; (b)  $R = 2 \text{ k}\Omega$ ; (c)  $V = 2 \text{ V}$ ; (d)  $I = 50 \text{ mA}$
- 1.3** (a)  $V = 2 \text{ V}$ ,  $P = 4 \text{ mW}$ ; (b)  $R = 50 \text{ k}\Omega$ ,  $P = 20 \text{ mW}$ ; (c)  $I = 100 \text{ mA}$ ,  $R = 10 \text{ k}\Omega$ ; (d)  $V = 20 \text{ V}$ ,  $R = 200 \text{ k}\Omega$
- 1.5**  $990 \text{ k}\Omega$ ,  $190 \text{ k}\Omega$ ,  $90 \text{ k}\Omega$ ,  $10 \text{ k}\Omega$ ;  $9.9 \text{ k}\Omega$ ,  $9.09 \text{ k}\Omega$ ,  $5 \text{ k}\Omega$
- 1.7**  $2 \text{ V}$ ;  $667 \text{ k}\Omega$ ;  $1.93 \text{ V}$  and  $2.07 \text{ V}$ ;  $700 \text{ k}\Omega$  and  $633 \text{ k}\Omega$
- 1.9**  $0.96 \text{ V}$ ; shunt the  $1\text{-k}\Omega$  resistor with  $15.67 \text{ k}\Omega$ ; add series  $20 \Omega$
- 1.14**  $2 \text{ k}\Omega$ ;  $2.5 \text{ k}\Omega$ ;  $0.1 \sin \omega t \text{ mA}$
- 1.16**  $0.05 \text{ mA}$
- 1.17**  $I_1 = 0.75 \text{ mA}$ ;  $I_2 = 0.5 \text{ mA}$ ;  $I_3 = 1.25 \text{ mA}$ ;  $2.5 \text{ V}$
- 1.19**  $2 \text{ V}$
- 1.22** (a)  $1 \text{ k}\Omega$ ; (b)  $-j265 \text{ k}\Omega$ ;  $-j159\Omega$ ;  $-j0.016\Omega$ ; (c)  $-j265 \text{ M}\Omega$ ;  $-j159 \text{ k}\Omega$ ;  $-j15.9\Omega$ ; (d)  $j3.77\Omega$ ;  $j6.28 \text{ k}\Omega$ ;  $j62.8 \text{ M}\Omega$ ; (e)  $j0.377 \text{ m}\Omega$ ;  $j0.628\Omega$ ;  $j6.28 \text{ k}\Omega$
- 1.23** (a)  $(1 - j15.9) \text{ k}\Omega$ ; (b)  $(717 + j450)\Omega$ ; (c)  $(9.96 - j0.626) \text{ k}\Omega$ ; (d)  $(10^5 + j628)\Omega$
- 1.25**  $3 \text{ V}$ ;  $3 \text{ mA}$ ;  $1 \text{ k}\Omega$ ; (b)  $0.5 \text{ V}$ ;  $50 \mu\text{A}$ ;  $10 \text{ k}\Omega$
- 1.27**  $55.2 \Omega$
- 1.30** (a)  $2\%$ ;  $9\%$ ; (b)  $1\%$ ;  $8\%$ ; (c)  $9\%$ ;  $0.4\%$ ;  $0.5 \text{ mA}$ ; (d)  $9\%$ ;  $1\%$ ;  $6.67 \text{ mA}$
- 1.33** (a)  $165 \text{ V}$ ; (b)  $24 \text{ V}$ ; (c)  $311 \text{ V}$ ; (d)  $311 \text{ kV}$
- 1.35**  $0 \text{ V}$ ;  $-1 \text{ V}$ ;  $+1 \text{ V}$ ;  $2 \text{ kHz}$
- 1.37**  $2\%$  lower
- 1.39** 0; 101; 1101; 10000; 111111
- 1.42** (b)  $b_N$ ;  $b_1$ ; (c)  $0.996 \text{ mA}$ ;  $3.91 \mu\text{A}$
- 1.43**  $7.056 \times 10^5$  bits per second
- 1.44** 66
- 1.45** (a)  $100 \text{ V/V}$ ;  $40 \text{ dB}$ ;  $1000 \text{ A/A}$ ;  $60 \text{ dB}$ ;  $10^5 \text{ W/W}$ ;  $50 \text{ dB}$ ; (b)  $10^5 \text{ V/V}$ ;  $100 \text{ dB}$ ;  $1000 \text{ A/A}$ ;  $60 \text{ dB}$ ;  $10^8 \text{ W/W}$ ;  $80 \text{ dB}$ ; (c)  $5 \text{ V/V}$ ;  $14 \text{ dB}$ ;  $500 \text{ A/A}$ ;  $54 \text{ dB}$ ;  $2500 \text{ W/W}$ ;  $34 \text{ dB}$
- 1.47**  $2.8 \text{ V}_{\text{rms}}$ ;  $14 \text{ mV}_{\text{rms}}$ ;  $6.4 \text{ V}_{\text{rms}}$ ;  $32 \text{ mV}_{\text{rms}}$ ;  $9.9 \text{ V}_{\text{rms}}$ ;  $50 \text{ mV}_{\text{rms}}$
- 1.49**  $38.4 \text{ dB}$ ;  $71.4 \text{ dB}$ ;  $85 \text{ mV}$ ;  $0.1 \text{ W}$
- 1.51**  $0.69 \text{ V}$ ;  $-3.2 \text{ dB}$ ;  $78.4 \text{ dB}$ ;  $37.6 \text{ dB}$
- 1.52**  $412.7 \text{ V/V}$
- 1.54** 4;  $16.37 \text{ V}$
- 1.56** (a)  $400 \text{ V/V}$ ; (b)  $40 \text{ k}\Omega$ ;  $2 \times 10^4 \text{ A/A}$ ;  $8 \times 10^6 \text{ W/W}$ ; (c)  $500 \Omega$ ; (d)  $750 \text{ V/V}$ ; (e) (i)  $100 \text{ k}\Omega$ ; (ii)  $100 \Omega$ ; (iii)  $484 \text{ V/V}$
- 1.58**  $1.1 \text{ mA}$ ;  $10 \text{ k}\Omega$

- 1.59** 4.95 A/A; 13.9 dB; 4.9 V/V; 13.8 dB; 24.3 W/W; 27.7 dB  
**1.60** 13.3 V/V  
**1.66** 683.3 V/V; 56.7 dB; 3.333 A/A; 70.5 dB;  $2.34 \times 10^6$  W/W; 127.4 dB  
**1.70** 4 MHz; 0.8 V/V  
**1.72** 57 nF  
**1.75**  $0.51/CR$   
**1.77** 0.8 kΩ; 3.98 kΩ; 8 nF at node B  
**1.81** 90 kΩ; 6.61 kΩ; 27.9 mA/V  
**1.82**  $R_2/(R_1 + R_2)$   
**1.83** 15.9 ms; 15.9 μs; -0.04 dB; 10 Hz and 10 kHz

## Chapter 2

- 2.1** 8; 14  
**2.2** 2502.5 V/V  
**2.3** -1 V; 1750 V/V  
**2.5**  $10^4$  V/V  
**2.9** (a) -6 V/V; 15 kΩ; (b) -6 V/V; 15 kΩ; (c) -6 V/V; 15 kΩ; (d) -6 V/V; 15 kΩ  
**2.12** (a) -2 V/V; (b) -10 V/V; (c) -0.5 V/V; (d) -50 V/V; (e) -5 V/V  
**2.14**  $R_1 = 1 \text{ k}\Omega$ ;  $R_2 = 5 \text{ k}\Omega$   
**2.18** 3 mA;  $R_1 = 2 \text{ k}\Omega$ ;  $R_2 = 20 \text{ k}\Omega$   
**2.19**  $\pm 2x\%$ ; -98 V/V to -102 V/V  
**2.21** 1.49 kΩ; 5.88 kΩ  
**2.23**  $\pm 2 \text{ mV}$   
**2.27** (b)  $R_1 = 1 \text{ k}\Omega$ ;  $R_2 = 30 \text{ k}\Omega$ ; 589 V/V  
**2.30** (a) 41.67 kΩ; (b) 111.1 kΩ; (c) 666.7 kΩ  
**2.32**  $-\frac{R_2}{R_1} \left( 1 + \frac{R_4}{R_3} + \frac{R_4}{R_2} \right)$   
**2.34** (a) 0.1 mA; 0.1 mA; 10 mA; 10.1 mA; -1 V; (b) 693 kΩ; (c)  $I_L = 10.1 \text{ mA}$ ;  $-6.05 \text{ V} \leq V_O \leq -2.01 \text{ V}$   
**2.37**  $R_1 = 100 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $R_3 = 1.02 \text{ k}\Omega$ ; -2.48 V/V  
**2.40**  $R_1 = 6 \text{ k}\Omega$ ;  $R_2 = 1.5 \text{ k}\Omega$ ;  $R_3 = 1 \text{ k}\Omega$ ;  $R_f = 6 \text{ k}\Omega$   
**2.44**  $R_f = 5.33 \text{ k}\Omega$   
**2.45** (a)  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 40 \text{ k}\Omega$ ; (b)  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 90 \text{ k}\Omega$ ; (c)  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 200 \text{ k}\Omega$ ; (d)  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 990 \text{ k}\Omega$   
**2.47** 100 kΩ; no  
**2.50**  $\frac{1 + R_2/R_1}{1 + R_3/R_4}$   
**2.55**  $\frac{1}{1 + 1/A}$ ; 0.999, -0.1%; 0.990, -1%; 0.909, -9.1%  
**2.58** 1980 V/V

- 2.59** 9.09 V/V; 81 k $\Omega$  in parallel with  $R_1$ ; 9.52 V/V; 10.52 V/V
- 2.62** 0 V  $\leq v_o \leq +2$  V; 0.1 V
- 2.63** 10 V/V; 10 k $\Omega$ ; 0.0091 V/V; 66.8 dB
- 2.68** (a) 1 V/V; 0 V/V; (b)  $-5$  V  $\leq v_{lcm} \leq +5$  V; (c) 10 V/V; 0 V/V;  $-3$  V  $\leq v_{lcm} \leq +3$  V
- 2.69** 1 M $\Omega$ ; 756  $\Omega$ ; 6.8 k $\Omega$
- 2.73**  $2v_{ld} + 0.01 \frac{(3 - 6x)}{(1 + x - x^2)}$ ;  $-60$  mV; increase 100  $\Omega$
- 2.75** (a)  $-0.05$  V  $\leq v_{lcm} \leq +0.05$  V; (b)  $-5$  V  $\leq v_{lcm} \leq +5$  V
- 2.76** (a) 0 dB; (b)  $20\log(1 + R_2/R_1)$
- 2.79** (b) 4 V/V; (c) 4 V<sub>p-p</sub>; 1.414 V<sub>rms</sub>
- 2.81** (a) 1.59 kHz; (c) increase by  $10\times$
- 2.83** 1 MHz; 0.159  $\mu$ s
- 2.84** 10 k $\Omega$ ; 10 nF; 10 kHz
- 2.88**  $R_1 = 10$  k $\Omega$ ;  $R_2 = 100$  k $\Omega$ ;  $C_2 = 15.9$  pF; 2 MHz
- 2.92**  $R_1 = 2$  k $\Omega$ ;  $R_2 = 200$  k $\Omega$ ;  $C = 79$  pF; 20 kHz
- 2.94** 7.3 mV
- 2.96** 27 mV; 30 mV
- 2.98** (a) 100 nA into the amplifier; (b)  $-5$  mV; (c) 10 nA
- 2.100** 1.01 k $\Omega$ ; 100 k $\Omega$ ; 100 k $\Omega$ ; 15.8 nF; 1.6 nF
- 2.102** 609 mV; 303 mV; 9 mV
- 2.104** (a) 0.2 V; (b) 0.3 V; (c) 10 k $\Omega$ ; 20 mV; (d) 0.12 V
- 2.106** (a) 9.9 k $\Omega$ ; (b) 0.222 V
- 2.108** 200,000 V/V; 100 Hz; 20 MHz
- 2.110** (a) 50 Hz; 10 MHz; (b) 100 Hz; 20 MHz; (c) 10 kHz; 18 MHz; (d) 1 MHz; 1 GHz; (e) 2.5 kHz; 500 MHz
- 2.112** 800 kHz; 84 kHz; 7.6 MHz
- 2.114** 10 V/V
- 2.116** 183 MHz
- 2.121** 100 mV
- 2.124** 4 V/ $\mu$ s
- 2.126** 6.37 MHz
- 2.127** (a) 318.3 kHz; (b) 0.795 V; (c) 2 MHz; (d) 1 V

## Chapter 3

- 3.2**  $2.2 \times 10^6$  cm $^{-3}$
- 3.4**  $2 \times 10^{18}$  cm $^{-3}$ ; 112.5 cm $^{-3}$
- 3.7** (a)  $11.4 \times 10^9$   $\Omega$ ; (b) 5 k $\Omega$ ; (c) 50  $\Omega$ ; (d) 15.63 k $\Omega$ ; (e) 0.14  $\Omega$
- 3.9** 8  $\mu$ m
- 3.11** 0.864 A/cm $^2$
- 3.13** 778 mV; 0.2  $\mu$ m; 0.1  $\mu$ m; 0.1  $\mu$ m;  $1.6 \times 10^{-15}$  C

- 3.15** 0.8 pC  
**3.17** 59.6 mV  
**3.20** 0.626  $\mu\text{m}$ ;  $9.1 \times 10^{-15}$  C  
**3.23**  $1.57 \times 10^{-17}$  A; 1.88 mA  
**3.24** 4.46  
**3.26** 10.42 mA; 41.7 mA  
**3.28** 0.23 pF  
**3.30** 0.25 pF; 64.8 ps

## Chapter 4

- 4.1** (a) 0 A; -1.5 V; (b) 0.75 A; 0 V  
**4.3** (a) 2 V; 5.5 mA; (b) 1 V; 4 mA  
**4.7** (a) 0 V; 2 mA; (b) -1.5 V; 0 mA  
**4.9** 4.2 k $\Omega$ ; 169.7 V  
**4.11** 25 mA; 12.5 mA  
**4.14**  $V = +3$  V  $\Rightarrow$  red ON, green OFF;  $V = 0$  V  $\Rightarrow$  red OFF, green OFF;  $V = -3$  V  $\Rightarrow$  red OFF, green ON  
**4.15**  $-7 \text{ V} \leq v_I \leq 8 \text{ V}$   
**4.17** 1.95 A; 10 V  
**4.19** 0.461 V;  $1.45 \times 10^{12} I_s$   
**4.21** 1.49 mA; 54.6 mA; 0.67 mA; 18.3  $\mu\text{A}$ ; 17.3 mV  
**4.23** (a)  $6.91 \times 10^{-15}$  A; 73.8 mA; (b)  $6.91 \times 10^{-16}$  A; 7.38 mA; (c)  $1.27 \times 10^{-13}$  A; 1.36 A; (d)  $6.91 \times 10^{-17}$  A; 0.738 mA; (e)  $3.78 \times 10^{-16}$  A; 4.04 mA  
**4.25** Decrease by 17.3 mV  
**4.27** 87.7 mV; 5.16 mA  
**4.31** 50° C; 6 W; 8.33° C/W  
**4.33** 230 mV independent of current and temperature  
**4.35** 0.664 V  
**4.38** (a) 0.767 mA; (b)  $5.3 \times 10^{-16}$  A; (c) 0.805 mA  
**4.41** (a) -4.3 V; 0.93 mA; (b) 5 V; 0 A; (c) 4.3 V; 0.93 mA; (d) -5 V; 0 A  
**4.43** (a) 1.3 mA; 0 V; (b) 0 mA; -1.675 V  
**4.45** 4.23 k $\Omega$ ; 169.7 V  
**4.47** 14.71 V; 3.61 V  
**4.49** +22.1 % or -18.1 %; +2.38 mV or -2.63 mV  
**4.53** 0 V/V; 0.001 V/V; 0.01 V/V; 0.1 V/V; 0.5 V/V; 0.6 V/V; 0.9 V/V; 0.99 V/V  
**4.54** (a) 0 V/V; 0.167 V/V; 0.667 V/V; 0.952 V/V; 0.995 V/V; 0.9995 V/V; (b)  $|\Delta v_D| < 2.5 \text{ mV}$ ;  $I \geq 5 \mu\text{A}$ ; (c) 1 V; 1.005 V;  $i_{D1} = i_{D4} = 0.45$  mA;  $i_{D2} = i_{D3} = 0.55$  mA  
**4.59** 470  $\Omega$ ; 7.39 mA; 11.09 mW; 1.5 mW; +6.8 mV; -3.4 mV; -6.8 mV; -13.6 mV  
**4.62** 47.6 mV  
**4.64** (a) 9.825 V; (b) 207  $\Omega$ ; (c) 33 mV/V;  $\pm 1.65\%$ ; (d) -6.77 V/A; -1.35%; (e) 70.9 mA; 732 mW

**4.67** 0.441 V**4.69** 13.44 V; 48.4%; 8.3 V; 16.6 mA**4.71** (a) 10.1:1; (b) 4.2:1; (c) 8.2**4.73** 30.4 V (45 V with 1.5× safety factor)**4.75** (i) 333.3  $\mu$ F; (ii) 3333  $\mu$ F; (a) (i) 12.77 V; (ii) 13.37 V; (b) (i) 7.1%; (ii) 2.24%; (c) 384 mA; (ii) 1214 mA; (d) (i) 742 mA; (ii) 2.4 A**4.78** (a) 9.7 V; (b) 542  $\mu$ F; (c) 25.7 V (38.5 V with 1.5× safety factor); (d) 739 mA; (e) 1.42 A**4.81** 10.74 V; 23.5  $\mu$ s; 4.913 A**4.83** (a) 1 V; 2 V; 2.7 V; (b) 3 V; 6 V; 6.7 V; (c) 0 V; 0 V; -13 V; (d) 0 V; 0 V; -13 V**4.86** -7.07 V**4.89** 0.70 V <  $V_R$  < 2.87 V**4.91** (a) 80  $\Omega$ ; (b) 120  $\Omega$ 

## Chapter 5

**5.2** 0.16 fC**5.4** (a) 0.5; (b) 0.5; (c) 1.0; (d) 0.5**5.5** 1.3 V to 0.62 V; 1.3  $\mu$ m**5.7** 1.85  $\mu$ m**5.10** (a)  $8.625 \times 10^{-3}$  pF/ $\mu$ m<sup>2</sup>, 388  $\mu$ A/V<sup>2</sup>; (b) 0.2 V, 0.7 V, 0.2 V; (c) 0.39 V, 0.89 V**5.13** 96.2  $\Omega$ , 19.2 mV; 80**5.16** 1.5 V; 500  $\Omega$  to 100  $\Omega$ **5.18** 2 mA/V<sup>2</sup>, 0.4 V**5.19** 1.07  $\mu$ m**5.20** 0.4 V; 5; 0.25 mA; 0.6 V, 0.45 mA**5.22** 2.5 k $\Omega$  to 125  $\Omega$ ; (a) 5 k $\Omega$  to 250  $\Omega$ ; (b) 1.5 k $\Omega$  to 62.5  $\Omega$ ; 2.5 k $\Omega$  to 125  $\Omega$ **5.28** (a) 2%; (b) 4%**5.29** 100 k $\Omega$ , 20 V, 0.05 V<sup>-1</sup>**5.32** 109  $\mu$ A; 9%; double  $L$  to 2  $\mu$ m**5.35** 15 V; 1.5  $\mu$ m**5.37** 8  $\mu$ A; 12  $\mu$ A; 13.13  $\mu$ A; 13.75  $\mu$ A; 15  $\mu$ A**5.40** 1.6 V, saturation region; 0.4 V, triode region**5.44** 0.045 mA, 20 k $\Omega$ , 10 k $\Omega$ ; 31.1 k $\Omega$ **5.47** 8 k $\Omega$ **5.49** 2.25  $\mu$ m, 0.56  $\mu$ m, 4 k $\Omega$ **5.51** 0.454 mA, +7.28 V; circuit is quite tolerant to variations in device parameters.**5.53** 44.4, 1.25 k $\Omega$ **5.55** (a) -0.6 V; (b) -0.816 V; (c) -1.5 V; (d) +0.6 V; (e) +1.5 V; (f) +0.6 V; (g) +1.5 V; (h) -0.6 V**5.58** (a) 360  $\mu$ A, 1 V; (b) 160  $\mu$ A, 0.8 V; (c) 1 V, 360  $\mu$ A

**5.60** (a) 0.5 V, 0.5 V,  $-0.723$  V; (b) 0.4 V, 0.6 V,  $-0.745$  V

**5.62** 488 million transistors

**5.63** 1 V to 1.69 V; 3.74 V

**5.68** 0.3 mA, 0.416 mA, 0.424 mA, 0.48 mA; each current value is doubled; for  $v_{DS} = 2$  V,  $i_D = 0.408$  mA, for  $v_{DS} = 3$  V,  $i_D = 0.412$  V, for  $v_{DS} = 10$  V,  $i_D = 0.44$  mA

## Chapter 6

**6.2**  $3.7 \times 10^{-17}$  A;  $1.87 \times 10^{-16}$  A; 5:1

**6.4** 0.276 V

**6.7** 0.18 mA; 0.605 V

**6.12** 0.5 mA  $\rightarrow$  2mA; 0.51 mA  $\rightarrow$  2.01 mA; 20 mW

**6.14** 990  $\mu$ A, 99, 0.99; 980  $\mu$ A, 49, 0.98; 950  $\mu$ A, 19, 0.95

**6.18** 437 k $\Omega$ ; 8 k $\Omega$

**6.22**  $-1$  V; 0.41 mA;  $-0.668$  V

**6.25** 238 mA;  $6 \times 10^{-14}$  A; 87 times

**6.28** (a) 1 mA,  $-0.7$  V; (b)  $-2$  V; (c) 1 V, 1 mA; (d) 0.77 mA,  $-2$  V

**6.30** 2.3 k $\Omega$ ; 20; 100; 200

**6.34**  $R_E = 1.62$  k $\Omega$ ,  $R_C = 3$  k $\Omega$

**6.39** (a) 632 mV; (b) 0.69 mA, 5.77 mA

**6.42** 0.1 mA, 0.11 mA;  $-8.16$  V;  $+22$  mV/ $^{\circ}$ C;  $-7.06$  V

**6.43** 200 k $\Omega$ ; 100 V; 20 k $\Omega$

**6.47** 100; 80; 1.18 mA

**6.48** (a) 1.3 V; (b) 1.64 V; (c) 5.5 V

**6.51** (a) 1.3 V, 3.7 V; (b) 1 V, 4 V; (c) 0 V, 5 V

**6.53**  $-1.7$  V,  $+1.7$  V;  $-0.7$  V,  $+0.7$  V;  $+0.3$  V,  $-0.3$  V;  $-1.17$  V;  $-1.5$  V;  $-2$  V,  $+2$  V; 0.55 V;  $-0.15$  V,  $+0.15$  V; 1.08 V

**6.55**  $R_1 = 35$  k $\Omega$ ,  $R_2 = 15$  k $\Omega$ ; 0.078 mA; 4.22 V

**6.56** 0.3 V; 0.003 mA; 0.15 mA; 0.147 mA;  $-1.03$  V; 49; 0.98

**6.58**  $+0.41$  V,  $+1.11$  V;  $-1.15$  V;  $+1.2$  V,  $+1.9$  V,  $-1.9$  V; 204

**6.60** 1.86 V, 1.16 V, 1.85 V; 2.14 V, 1.44 V, 1.64 V; 2.4 V, 1.7 V, 1.9 V

**6.62** (a)  $-0.915$  V,  $+1.218$  V; (b)  $+1.258$  V, 0.49 mA; (c)  $-0.9$  V,  $-0.2$  V,  $+1.4$  V; (d)  $+1.7$  V,  $-0.9$  V; (e)  $+1$  V,  $+1.7$  V,  $-0.9$  V

**6.63** 50 k $\Omega$ , 4 k $\Omega$ , 4 k $\Omega$ ; 0.85 mA to 0.98 mA with 0.95 mA nominal;  $-1.6$  V to  $-1.1$  V with  $-1.2$  V nominal.

**6.64** 1.74 k $\Omega$ ; transistor saturates and  $V_C = 2.8$  V

**6.66** (a) 0 V,  $+0.7$  V,  $-0.725$  V,  $-1.425$  V,  $+1.1$  V; (b)  $+0.23$  V,  $+0.93$  V,  $-1$  V,  $-1.7$  V,  $+1.47$  V

**6.68** (a) 0 V, 0 V; (b)  $-1.8$  V,  $-1.1$  V; (c)  $+2.2$  V,  $+1.5$  V; (d)  $+3$  V, 2.3 V

**6.69** (a)  $+0.8$  V, 2.3; (b)  $+2.07$  V, 3.2; (c)  $V_{C3} = 2.044$  V,  $V_{C4} = 1.54$  V,  $\beta_{\text{forced3}} = 0.8$ ,  $\beta_{\text{forced4}} = 6.4$ .

## Chapter 7

**7.1** A: (0.5 V, 3 V); B: (0.69 V, 0.19 V)

**7.2**  $12\text{ k}\Omega$ ;  $6\text{ k}\Omega$

**7.4** 0.214 V; 0.716 V

**7.6** 0.5 V; 8

**7.10**  $-80\text{ V/V}$ ; 0.7 V; 8.8 mV

**7.12** 0.75 V; 0.45 V;  $-90\text{ V/V}$

**7.15**  $-40\text{ V/V}$

**7.19** (a)  $108\text{ V/V}$ ; (b) 1.5 V; (c)  $3\text{ k}\Omega$ ; (d) 0.673 V; (e) 0.3 V; (f)  $0.1 \sin \omega t$ , mA; (g) 0.005 mA,  $0.001 \sin \omega t$ , mA; (h)  $5\text{ k}\Omega$

**7.24** (a) 0.1 mA, 0.5 V; (b) 1 mA/V; (c)  $-15\text{ V/V}$ ; (d)  $-0.225 \sin \omega t$ , V, 0.275 V, 0.725 V; (e) 1.9%

**7.25** (a) 0.2 mA, 0.44 V; (b) 2 mA/V; (c)  $-13.6\text{ V/V}$ ; (d)  $25\text{ k}\Omega$ ,  $-10.7\text{ V/V}$

**7.27** (a) 2 mA/V,  $20\text{ k}\Omega$ ; (b) 2.9 mA/V,  $10\text{ k}\Omega$

**7.29**  $12\text{ k}\Omega$ ;  $10\text{ }\mu\text{m}$ ; 0.75 V

**7.31**  $-26.1\text{ V/V}$ ; 1.25 V,  $-38.3\text{ V/V}$

**7.32** NMOS: 0.91 mA/V,  $25\text{ k}\Omega$ , 0.22 V; PMOS: 0.447 mA/V,  $30\text{ k}\Omega$ , 0.447 V

**7.36** 16 mA/V,  $6.25\text{ k}\Omega$ ,  $61.9\text{ }\Omega$ ; 1.6 mA/V,  $62.5\text{ k}\Omega$ ,  $618.8\text{ }\Omega$

**7.37** 20 mA/V;  $50\text{ }\Omega$ ;  $5\text{ k}\Omega$ ; 0.5 V

**7.38** 0.5 mA; 80

**7.48** 0.5 V;  $100\text{ }\Omega$ ; 100 V/V

**7.49** 0.005 V, 0.001 mA

**7.54** 1 V;  $5\text{ k}\Omega$ ;  $3.33\text{ k}\Omega$ ;  $-30.8\text{ V/V}$ , 9.7 mV; 7.5 mV

**7.55**  $V_A = 20\text{ V}$ ;  $-800\text{ V/V}$ ;  $V_A = 120\text{ V}$ ;  $-4800\text{ V/V}$

**7.57**  $17.2\text{ k}\Omega$ ;  $18\text{ k}\Omega$ ; 90 V/V

**7.59** 82.6 V/V; 9086 A/A

**7.60**  $190\text{ k}\Omega$ ; 111 V/V;  $55.6\text{ }\Omega$

**7.61** 1000 V/V; 250 V/V

**7.64**  $-20\text{ V/V}$

**7.66** 1.5 mA/V; 0.15 mA;  $-7.5\text{ V/V}$

**7.68**  $10\text{ k}\Omega$ ;  $10\text{ k}\Omega$ ;  $-160\text{ V/V}$ ;  $-80\text{ V/V}$ ;  $-40\text{ V/V}$ ; 10 mV; 0.4 V

**7.71**  $200\text{ }\Omega$

**7.73** 5 mA/V;  $4\text{ k}\Omega$ ;  $50\text{ }\Omega$

**7.75**  $600\text{ }\Omega$ ; 0.375 mA;  $-7.4\text{ V/V}$ ; 0.74 V

**7.77**  $0.2\text{ k}\Omega$ ;  $5.6\text{ V/V}$ ; 0.64

**7.79** 0.5 mA; 25 V/V

**7.81** 8 V/V; 50 mV; 0.4 V

**7.83** 2.5 mA; 2.75 mA; 2.25 mA; 0.55 V

**7.85** (a)  $20.7\text{ k}\Omega$ , 0.67 V/V, 0.65 V/V; (b) 0.615 V, 0.4 V; (c) 1 V/V,  $104\text{ }\Omega$ , 0.59 V/V

**7.87** 1 V/V;  $105\text{ }\Omega$ ; 0.9 V/V

**7.91** 27.5 V/V, 41.2 V/V, 55.6 V/V, 57.1 V/V, 55.6 V/V; 0.325 mA

- 7.92**  $22\text{ M}\Omega$ ;  $18\text{ M}\Omega$ ;  $15\text{ k}\Omega$ ;  $15\text{ k}\Omega$ ;  $2.7\text{ V}$  above
- 7.94**  $5.07\text{ V}$ ;  $1.27\text{ mA}$  to  $2.48\text{ mA}$ ;  $620\text{ }\Omega$ ;  $0.91\text{ mA}$  to  $1.5\text{ mA}$
- 7.96**  $2\text{ V}$ ;  $2.4\text{ V}$ ;  $1.2\text{ mA}$
- 7.97**  $R_S = 5\text{ k}\Omega$ ;  $R_D = 7.5\text{ k}\Omega$
- 7.101** (a)  $1.25\text{ V}$ ; (b)  $1.85\text{ V}$
- 7.102**  $9.5\text{ k}\Omega$
- 7.103**  $1.3\text{ k}\Omega$ ;  $1.7\text{ M}\Omega$ ;  $13\text{ M}\Omega$
- 7.106**  $6.2\text{ k}\Omega$ ;  $6.2\text{ k}\Omega$ ;  $100\text{ k}\Omega$ ;  $75\text{ k}\Omega$ ;  $3.6\text{ V}$ ;  $2.9\text{ V}$ ;  $6.1\text{ V}$ ;  $0.46\text{ mA}$
- 7.107**  $6.2\text{ k}\Omega$ ;  $6.2\text{ k}\Omega$ ;  $100\text{ k}\Omega$ ;  $82\text{ k}\Omega$ ;  $0.5\text{ mA}$ ;  $0.49\text{ mA}$ ;  $3.8\text{ V}$ ;  $6\text{ V}$
- 7.109**  $R_E = 1.5\text{ k}\Omega$ ;  $R_C = 2.4\text{ k}\Omega$ ;  $R_B = 7.5\text{ M}\Omega$ ;  $\beta = \infty$ :  $0.52\text{ mA}$ ,  $0\text{ V}$ ,  $0.25\text{ V}$ ;  $\beta = 50$ :  $0.48\text{ mA}$ ,  $-0.07\text{ V}$ ,  $0.35\text{ V}$
- 7.111**  $R_C = 3.3\text{ k}\Omega$ ;  $R_B = 120\text{ k}\Omega$ ;  $0.56\text{ mA}$ ,  $0.85\text{ V}$
- 7.113**  $0.505\text{ mA}$ ;  $160\text{ k}\Omega$
- 7.116**  $4.6\text{ k}\Omega$ ;  $+0.4\text{ V}$
- 7.117**  $-26.7\text{ V/V}$
- 7.119** (a)  $3\text{ k}\Omega$ ; (b)  $3\text{ k}\Omega$ ; (c)  $0.135\text{ V}$ ,  $1.62\text{ V}$ ; (d)  $4.6\text{ k}\Omega$ ,  $-18.4\text{ V/V}$
- 7.121** (a)  $9.5\text{ k}\Omega$ ; (b)  $12.5\text{ k}\Omega$ ;  $10\text{ M}\Omega$ ; (b)  $2\text{ mA/V}$ ,  $100\text{ k}\Omega$ ; (c)  $-9.6\text{ V/V}$ ; (d)  $0.946\text{ V/V}$ ,  $473\text{ }\Omega$ ; (e)  $0.6\text{ V}$
- 7.125**  $0.47\text{ mA}$ ;  $4.7\text{ k}\Omega$ ;  $-30.4\text{ V/V}$
- 7.128**  $R_B = 91\text{ k}\Omega$ ;  $R_C = 22\text{ k}\Omega$ ;  $0.2\text{ mA}$ ;  $-176\text{ V/V}$ ,  $-29.7\text{ V/V}$
- 7.129** (a)  $11.5\text{ k}\Omega$ ; (b)  $12.5\text{ k}\Omega$ ; (c)  $-31.7\text{ V/V}$
- 7.131**  $27.5\text{ k}\Omega$ ;  $-9.8\text{ V/V}$ ;  $20.5\text{ mV}$ ;  $0.2\text{ V}$
- 7.135**  $163.4\text{ k}\Omega$ ;  $0.6\text{ V/V}$ ;  $52.9\text{ A/A}$ ;  $789\text{ }\Omega$
- 7.136** (a)  $1.7\text{ mA}$ ,  $68.4\text{ mA/V}$ ,  $0.0145\text{ k}\Omega$ ,  $1.46\text{ k}\Omega$ ; (b)  $148.3\text{ k}\Omega$ ,  $0.93\text{ V/V}$ ; (c)  $18.21\text{ k}\Omega$ ,  $0.64\text{ V/V}$
- 7.137** (a)  $0.1\text{ mA}$ ,  $5\text{ mA}$ ,  $1.5\text{ V}$ ,  $0.8\text{ V}$ ; (b)  $0.995\text{ V/V}$ ,  $101.5\text{ k}\Omega$ ; (c)  $456\text{ k}\Omega$ ,  $0.9975\text{ V/V}$ ; (d)  $0.82\text{ V/V}$ ; (e)  $0.814\text{ V/V}$

## Chapter 8

- 8.2**  $66\text{ k}\Omega$ ;  $6\text{ }\mu\text{m}$ ;  $0.2\text{ V}$ ;  $40\text{ k}\Omega$ ;  $+5\text{ }\mu\text{A}$
- 8.5**  $0.2\text{ V}$ ;  $100\text{ }\mu\text{A}$ ;  $0.2\text{ V}$ ;  $27\text{ k}\Omega$ ;  $81.5\text{ }\mu\text{A}$ ;  $100\text{ }\mu\text{A}$ ;  $118.5\text{ }\mu\text{A}$ ;  $137\text{ }\mu\text{A}$
- 8.7**  $5\text{ }\mu\text{m}$ ;  $20\text{ }\mu\text{m}$ ;  $12.5\text{ }\mu\text{m}$ ;  $3.125\text{ }\mu\text{m}$ ;  $6.25\text{ }\mu\text{m}$ ;  $15\text{ k}\Omega$ ;  $37.5\text{ k}\Omega$ ;  $30\text{ k}\Omega$
- 8.10**  $0.01\text{ mA}$ ;  $5\%$
- 8.14**  $1.013\text{ mA}$ ;  $2.28\text{ k}\Omega$ ;  $2.7\text{ V}$ ;  $+0.15\text{ mA}$
- 8.16** (a)  $I = 0.4\text{ mA}$ ; (b)  $I = 0.04\text{ mA}$ ; (a) and (b):  $V_1 = -0.7\text{ V}$ ,  $V_2 = +2\text{ V}$ ,  $V_3 = +0.7\text{ V}$ ,  $V_4 = -0.7\text{ V}$ ,  $V_5 = -1.7\text{ V}$
- 8.19**  $1.187\text{ V}$ ;  $0.113\text{ V}$ ;  $99.98\text{ }\mu\text{A}$ ;  $0.9998\text{ mA}$ ,  $-0.02\%$ ;  $0.3\text{ V}$
- 8.23**  $20\text{ }\mu\text{m}$ ;  $80\text{ }\mu\text{m}$ ;  $0.8\text{ }\mu\text{m}$ ;  $-0.6\%$
- 8.24**  $v_o/v_i = g_{m1}R_L (W_3/W_2)$
- 8.26** (a)  $800\text{ }\Omega$ ; (b)  $125\text{ }\Omega$

- 8.28**  $10\text{ k}\Omega$ ;  $-1200\text{ V/V}$ ;  $60\text{ k}\Omega$ ;  $0.1\text{ mA}$ ;  $-1200\text{ V/V}$ ;  $300\text{ k}\Omega$ ;  $-400\text{ V/V}$
- 8.29**  $40\text{ V/V}$ ;  $0.1\text{ mA}$ ;  $5\text{ }\mu\text{m}$
- 8.31**  $0.5\text{ }\mu\text{m}$ ;  $12.5$ ;  $0.1\text{ mA}$
- 8.33**  $0.25\text{ mA}$ ;  $2\text{ mA/V}$
- 8.35**  $2\text{ mA/V}$ ;  $13.5\text{ k}\Omega$ ;  $27\text{ V/V}$ ;  $14\text{ }\mu\text{m}$
- 8.37**  $0.146\text{ mA}$
- 8.40**  $40\text{ V/V}$ ;  $5.6\text{ }\mu\text{m}$ ;  $0.67\text{ mA/V}$ ;  $60\text{ k}\Omega$
- 8.41**  $0.75\text{ V}$ ;  $17.4$ ;  $69.4$ ;  $-14.5\text{ V/V}$
- 8.44** (a)  $0.95\text{ V}$ ,  $0.475\text{ }\mu\text{A}$ ,  $2.4\text{ V}$ ; (b)  $-86\text{ V/V}$ ,  $1.93\text{ V}$ ,  $22\text{ mV}$ ; (c)  $33.9\text{ k}\Omega$
- 8.46**  $50\text{ }\mu\text{A}$ ;  $4$ ;  $16$ ,  $16$
- 8.48** (a)  $0.125\text{ mA}$ ,  $0.125\text{ mA}$ ; (b)  $-999\text{ V/V}$ ; (c)  $-74.1\text{ V/V}$ ,  $13.3\text{ k}\Omega$ ; (d)  $-29.6\text{ V/V}$ ; (e)  $-0.5\text{ V}$  to  $+0.5\text{ V}$
- 8.49** (a)  $0.2\text{ mA}$ ; (b)  $100\text{ k}\Omega$ ,  $100\text{ k}\Omega$ ,  $50\text{ k}\Omega$ ; (c)  $6.25\text{ k}\Omega$ ,  $8\text{ mA/V}$ ; (d)  $6.25\text{ k}\Omega$ ,  $-400\text{ V/V}$ ,  $50\text{ k}\Omega$
- 8.50**  $21\text{ k}\Omega$ ;  $0.976\text{ A/A}$ ;  $840\text{ k}\Omega$ ;  $20.5\text{ V/V}$
- 8.52**  $40\text{ V/V}$ ;  $0.6\text{ }\mu\text{m}$
- 8.54**  $252\text{ k}\Omega$
- 8.56**  $1.4\text{ k}\Omega$ ;  $0.98\text{ A/A}$ ;  $10.2\text{ M}\Omega$ ;  $35.7\text{ V/V}$
- 8.59**  $0.1\text{ mA}$ ;  $12.2\text{ M}\Omega$ ;  $0.16\text{ }\mu\text{A}$
- 8.62**  $2\text{ V}$ ;  $0.5\text{ }\mu\text{m}$
- 8.63**  $-1600\text{ V/V}$
- 8.66**  $0.32\text{ }\mu\text{m}$ ;  $39.1$ ;  $0.7\text{ V}$ ;  $0.225\text{ mA}$ ;  $0.3\text{ V}$
- 8.68**  $1.6\text{ mA/V}$ ;  $640\text{ k}\Omega$ ;  $640\text{ k}\Omega$ ;  $320\text{ k}\Omega$ ;  $-512\text{ V/V}$
- 8.71**  $0.2\text{ V}$ ;  $0.5\text{ V}$  to  $0.8\text{ V}$
- 8.75**  $1.24\text{ M}\Omega$
- 8.78**  $-3.2 \times 10^4\text{ V/V}$
- 8.80**  $360\text{ }\mu\text{A}$ ;  $2.4\text{ mA/V}$ ;  $0.48\text{ mA/V}$ ;  $15\text{ k}\Omega$ ;  $0.8\text{ V/V}$ ;  $0.33\text{ k}\Omega$ ;  $0.72\text{ V/V}$
- 8.81**  $0.68\text{ V}$ ;  $1.1\text{ M}\Omega$
- 8.84**  $5\text{ M}\Omega$ ;  $+0.2\text{ }\mu\text{A}$ ;  $+0.1\%$
- 8.88**  $0.56\text{ V}$ ;  $1.12\text{ V}$ ;  $0.72\text{ V}$
- 8.93** (a)  $58.5\text{ k}\Omega$ ; (b)  $100\text{ M}\Omega$

## Chapter 9

- 9.1** (a)  $0.2\text{ V}$ ,  $0.6\text{ V}$ ; (b)  $-0.6\text{ V}$ ,  $0.08\text{ mA}$ ,  $0.08\text{ mA}$ ,  $+0.6\text{ V}$ ,  $+0.6\text{ V}$ ,  $0\text{ V}$ ; (c)  $-0.2\text{ V}$ ,  $0.08\text{ mA}$ ,  $0.08\text{ mA}$ ,  $+0.6\text{ V}$ ,  $+0.6\text{ V}$ ,  $0\text{ V}$ ; (d)  $-0.7\text{ V}$ ,  $0.08\text{ mA}$ ,  $0.08\text{ mA}$ ,  $+0.6\text{ V}$ ,  $+0.6\text{ V}$ ,  $0\text{ V}$ ; (e)  $1.0\text{ V}$ ; (f)  $-0.8\text{ V}$ ,  $-0.2\text{ V}$ ; (g)  $-0.2\text{ V}$  to  $1.0\text{ V}$
- 9.4**  $-0.283\text{ V}$  to  $+0.283\text{ V}$ ; At  $v_{id} = -0.283\text{ V}$ :  $v_s = 0.4\text{ V}$ ,  $v_{D1} = -0.1\text{ V}$ ,  $v_{D2} = -0.9\text{ V}$ ,  $v_o = -0.8\text{ V}$ ; At  $v_{id} = +0.283\text{ V}$ :  $v_s = +0.683\text{ V}$ ,  $v_{D1} = -0.9\text{ V}$ ,  $v_{D2} = -0.1\text{ V}$ ,  $v_o = +0.8\text{ V}$
- 9.7**  $0.365$ ;  $15$ ;  $1.1\text{ mA/V}$

- 9.9** 0.177 V; 400  $\mu$ A
- 9.11** (a)  $0.1V_{ov}$ ; (b) 0 V,  $0.338V_{ov}$ ,  $0.05V_{ov}$ ,  $0.005V_{ov}$ ;  $1.072V_{ov}$
- 9.13** 0.25 V; 0.5 mA; 5 k $\Omega$ ; 40
- 9.15** 0.14 V; 0.25 mA; 4.4 k $\Omega$ ; 25.5
- 9.16** (a) 0.426 mA/V; (b) 85  $\mu$ A; (c) 2 V; (d) 0.1 V; (e) 2.11 V
- 9.18** 2 $\times$
- 9.23** 4 k $\Omega$ ; 50, 50, 100, 12.5, 12.5, 100, 25; 0.1 mA, 0.1 mA, 0.2 mA, 0.1 mA, 0.1 mA, 0.2 mA, 0.2 mA; 0.6 V, 0.6 V, 0.6 V, 0.6 V, 0.6 V, 0.6 V, 0.6 V
- 9.26** -1.14 V; +1 V; +1 V
- 9.28** -0.56 V to +1.41 V
- 9.30** (a) -0.574 V, +0.4 V, +0.4 V; (b) -0.326 V to +0.674 V; (c) 5 mV
- 9.32** (a)  $V_{cc} - \frac{I}{2}R_C$ ; (b) 1.5 V; (c) 0.2 mA, 7.5 k $\Omega$ ;
- 9.36** 0.2 mA, 0.4 mA; 17.3 mV
- 9.38** 4 mA/V; 80 k $\Omega$
- 9.39** 0.2 mA; 20 k $\Omega$
- 9.42** Differential amplifier with a resistance  $R_e$  in each emitter;  $I = 0.5$  mA;  $R_e = 1.9$  k $\Omega$ ;  $R_C = 20$  k $\Omega$
- 9.43** (a) 0.2 mA, 15 k $\Omega$ , +1 V; (b) 50 k $\Omega$ ; (c)  $\pm 0.3$  V; (d) 1.1 V
- 9.49** 20 V/V
- 9.51** 20 V/V
- 9.52** 20 V/V; 101 k $\Omega$
- 9.53** 20 V/V; 101 k $\Omega$
- 9.55** 12 V/V;  $6 \times 10^{-4}$  V/V; 86 dB
- 9.57** (a) 0.94 V; (b) 107 k $\Omega$ ; (c) 0.93 V; (d) -2.26 V/V; (e) 0.12 V
- 9.58** 4%
- 9.59** 1  $\mu$ m; 102 dB
- 9.61** (a) 20 V/V; (b) 0.23 V/V; (c) 86.5; (d)  $-0.023 \sin 2\pi \times 60t + 0.2 \sin 2\pi \times 1000t$ , V
- 9.65** (a) 40 V/V; (b)  $5 \times 10^{-3}$  V/V, 78 dB; (c)  $1 \times 10^{-4}$  V/V; 112 dB
- 9.68** 1%
- 9.69**  $\frac{2}{3}I$  in  $Q_1$  and  $\frac{1}{3}I$  in  $Q_3$ ; 0.0125 V/V
- 9.72** 8 mV;  $\Delta V_t$ ; 8%
- 9.73** 1.6 mV, 1.6 mV, 4 mV; 7.2 mV; 4.6 mV
- 9.75** 2 mV
- 9.79** 1.25 mV
- 9.81** (a) 0.25; (b) 0.28
- 9.84** 1.6 k $\Omega$ ; 0.8 k $\Omega$ ; 2 k $\Omega$
- 9.86** 15 V/V
- 9.87** 1.25 mA/V; 30 k $\Omega$ ; 30 k $\Omega$ ; 18.8 V/V
- 9.89** 2.6 V
- 9.92** 1 mA/V; 44.4 k $\Omega$ ; 44.4 V/V; 44.4 k $\Omega$ ;

- 9.94** 25 k $\Omega$ ; 25 k $\Omega$ ; 8 mA/V; 200 V/V; 100 V/V
- 9.96** (a) +4 V; (b) +2.5 V; (c) +1.4 V; (d) +1.1 V
- 9.99** (a) 17.8, 17.8, 71.1, 71.1; (b) 0.6  $\mu$ m; (c) -0.4 V to +0.65 V; (d) 77 dB
- 9.101** 1 mA/V; 30 k $\Omega$ ; 30 V/V; 30 k $\Omega$ ; 0.984 k $\Omega$ ; 0.9836 A/A;  $5.56 \times 10^{-4}$  mA/V; 0.0167 V/V; 65.1 dB
- 9.103** 81 k $\Omega$
- 9.106** (a)  $|V_{ov}|$  is reduced by a factor of 2 and  $g_m$  increases by a factor of 20; (b) Both increase by a factor of 20; (c) increases by a factor 2 (except for  $V_{os}$  due to  $\Delta V_i$ ).
- 9.107** 120  $\mu$ A; 455 mV; 0.73 mV
- 9.110** 0.2 mA, 0.2 mA, 0.2 mA, 0.2 mA, 0.25 mA, 0.5 mA;  $1.61 \times 10^5$  V/V
- 9.111** 12.5 V/V; 40 k $\Omega$ ; 3300 A/A
- 9.113**  $R_5$ ; 7.37 k $\Omega$ ; reduced by a factor of 2; reduce  $R_4$  to 1.085 k $\Omega$ .
- 9.115** (a) 0.52 mA, 1.04 mA, 2.1 mA, 0 V; (b) 4 k $\Omega$ , 65.5  $\Omega$ ; (c) 8770 V/V

## Chapter 10

- 10.1**  $g_m = 2.6$  mA/V;  $g_{mb} = 0.6$  mA/V;  $r_o = 50$  k $\Omega$ ;  $C_{gs} = 23.7$  fF;  $C_{gd} = 3.1$  fF;  $C_{sb} = 4.2$  fF;  $C_{db} = 3.4$  fF;  $f_T = 15.4$  GHz
- 10.2** 12.7 GHz
- 10.6** 578.9 MHz; 5.79 MHz
- 10.10** 0.22 pF; 20 mA/V; 6 k $\Omega$ ; 100 MHz
- 10.14** 3.18 MHz
- 10.15** -40 V/V; 34.6 MHz; 127.3 GHz
- 10.18**  $100.1$  pF;  $-\frac{1000}{1+s C_{in} R_{sig}}$ ; 159 kHz; 159 MHz
- 10.21** 259 kHz; -27.8 V/V; changing  $R_L$ :  $R_L = 6.17$  k $\Omega$ ,  $|A_M| = 12.4$  V/V; changing  $R_{in}$ :  $R'_{sig} = 25$  k $\Omega$ ,  $R_{in} = 33.3$  k $\Omega$ ,  $|A_M| = 13.9$  V/V
- 10.22** -25 V/V; 49.7 MHz; 31.8 GHz
- 10.24** 31.83 fF; 286.5 fF; 20 MHz
- 10.26** -25 V/V; 254.6 MHz; 31.8 GHz
- 10.27** 61 pF; 522 kHz
- 10.30** -29.3 V/V; 988 kHz
- 10.33** 1 M $\Omega$
- 10.37** (a) 0.54 mA; (b) 21.6 mA/V, 4.63 k $\Omega$ ; (c) -10.8 V/V; (d) 4 k $\Omega$ , 2.14 k $\Omega$ ; (e) -7.4 V/V; (f) 14.37 pF; (g) 16.3 MHz
- 10.40** 39.8 MHz; 159 GHz
- 10.41** -41.7 V/V; 140 kHz
- 10.43** -80 V/V; 10.1 pF; 788 kHz; 652 kHz; the second estimate is more appropriate as it takes  $C_L$  into account.
- 10.45** 118 fF
- 10.48** -143 V/V; 3.2 MHz; 2.47 MHz; the second estimate as it takes  $C_L$  into account.

- 10.49**  $-50 \text{ V/V}$ ;  $479 \text{ kHz}$
- 10.50**  $8 \text{ V/V}$ ;  $159 \text{ MHz}$ ;  $5 \text{ MHz}$ ;  $5 \text{ MHz}$
- 10.53**  $14.4 \text{ fF}$
- 10.54**  $31.8 \text{ MHz}$
- 10.56**  $-913 \text{ V/V}$ ;  $5.76 \text{ MHz}$
- 10.58**  $0.2 \text{ V}$ ;  $0.2 \text{ mA}$ ;  $289.4 \text{ MHz}$ ;  $57.9 \text{ MHz}$ ;  $-99 \text{ V/V}$ ;  $2.9 \text{ MHz}$ ;  $287.1 \text{ MHz}$
- 10.61**  $-50 \text{ V/V}$ ;  $4 \text{ MHz}$
- 10.64**  $0.9 \text{ V/V}$ ;  $200 \Omega$ ;  $398 \text{ MHz}$ ;  $33.4 \text{ MHz}$ ,  $90.7 \text{ MHz}$ ;  $31.6 \text{ MHz}$
- 10.68**  $27 \text{ k}\Omega$ ;  $884 \text{ kHz}$ ;  $0.33 \text{ mA/V}$
- 10.69**  $0.96 \text{ V/V}$ ;  $2 \text{ GHz}$ ;  $740 \text{ MHz}$ ,  $4.6 \text{ GHz}$ ;  $740 \text{ MHz}$
- 10.70** (a)  $0.2 \text{ V}$ ,  $1 \text{ mA/V}$ ; (b)  $25 \text{ V/V}$ ; (c)  $212 \text{ MHz}$ ; (d)  $42.3 \text{ MHz}$
- 10.73**  $15.9 \text{ MHz}$ ;  $40 \text{ MHz}$
- 10.76**  $25 \text{ V/V}$ ;  $63.7 \text{ MHz}$ ;  $3.18 \text{ GHz}$ ;  $6.37 \text{ GHz}$
- 10.79** (a)  $-80 \text{ V/V}$ ,  $8.9 \text{ MHz}$ ,  $712 \text{ MHz}$ ; (b)  $-40 \text{ V/V}$ ,  $16.6 \text{ MHz}$ ,  $664 \text{ MHz}$
- 10.85** (a)  $2.5 \text{ M}\Omega$ ,  $-4000 \text{ V/V}$ ;  $107.6 \text{ MHz}$
- 10.86**  $20 \text{ V/V}$ ;  $1.33 \text{ MHz}$ ,  $19.9 \text{ MHz}$ ;  $1.33 \text{ MHz}$
- 10.88**  $50 \text{ V/V}$ ;  $4.6 \text{ MHz}$
- 10.89** (a)  $2500 \text{ V/V}$ ; (b)  $9.1 \text{ MHz}$
- 10.93**  $20 \text{ nF}$
- 10.95**  $8 \mu\text{F}$ ;  $89.5 \text{ Hz}$ ;  $10 \text{ Hz}$
- 10.96**  $-15.8 \text{ V/V}$ ;  $1.9 \text{ Hz}$ ;  $87.5 \text{ Hz}$ ;  $8 \text{ Hz}$ ;  $10.8 \text{ Hz}$ ;  $87.5 \text{ Hz}$
- 10.98**  $-31.6 \text{ V/V}$ ;  $C_s = 7 \mu\text{F}$ ;  $C_{C1} = 90 \text{ nF}$ ;  $C_{C2} = 0.4 \mu\text{F}$ ;  $90.9 \text{ Hz}$
- 10.99**  $C_E = 5 \mu\text{F}$ ;  $C_{C1} = 0.5 \mu\text{F}$ ;  $C_{C2} = 0.5 \mu\text{F}$ ;  $92.2 \text{ Hz}$ ;  $6 \mu\text{F}$
- 10.101**  $C_{C1} = 0.8 \mu\text{F}$ ;  $C_{C2} = 0.8 \mu\text{F}$ ;  $C_E = 9 \mu\text{F}$
- 10.102**  $141.4$

## Chapter 11

- 11.1**  $100$ ;  $99$ ;  $9.9 \times 10^{-3}$ ;  $99.89$ ;  $0.11\%$ ;  $91.7$ ;  $8.3\%$
- 11.2**  $0.01$ ;  $100$ ;  $10^4$
- 11.5**  $0.1$ ;  $990$ ;  $9.9$
- 11.8**  $1500 \text{ V/V}$ ;  $30 \text{ V/V}$ ;  $50$ ;  $49$ ;  $0.0327$
- 11.10**  $99$ ;  $9$
- 11.12**  $2000 \text{ V/V}$ ;  $0.0495 \text{ V/V}$
- 11.16**  $1000 \text{ V/V}$ ;  $0.099 \text{ V/V}$ ,  $1961 \text{ V/V}$
- 11.19**  $100 \text{ kHz}$ ;  $0.099 \text{ V/V}$
- 11.21** Three stages each with a closed-loop gain of  $10 \text{ V/V}$  and  $\beta = 0.099 \text{ V/V}$
- 11.22**  $0.089 \text{ V/V}$ ; for  $|v_s| \leq 0.45 \text{ V}$ ,  $v_o/v_s = 11.1 \text{ V/V}$ , for  $0.45 \text{ V} \leq |v_s| \leq 0.95 \text{ V}$ ,  $\Delta v_o / \Delta v_s = 10.1 \text{ V/V}$ , and for  $|v_s| \geq 0.95 \text{ V}$ ,  $v_o = \pm 10 \text{ V}$
- 11.24**  $90 \text{ k}\Omega$ ;  $100$ ;  $9.9 \text{ V/V}$ ;  $91 \text{ k}\Omega$
- 11.26** (a)  $4 \text{ k}\Omega$ ; (b)  $37.1$ ,  $4.87 \text{ V/V}$

**11.28** (a)  $0.9 \text{ k}\Omega$ ; (b)  $31.33, 9.7 \text{ V/V}, -3\%$ , make  $R_F = 933 \Omega$

**11.29** (a)  $1 + \frac{R_2}{R_1} = 11 \text{ V/V}$ ; (b)  $0.1 \text{ mA}, 0.3 \text{ mA}, +7.7 \text{ V}$ ; (c)  $23.2$ ; (d)  $10.55 \text{ V/V}$

**11.30** (a)  $0.95 \text{ k}\Omega$ ; (b)  $22.22, 19.1 \text{ V/V}$

**11.32**  $9.95 \text{ V/V}; 402 \text{ k}\Omega; 10 \Omega$

**11.35**  $10 \text{ V/V}; 1.001 \text{ M}\Omega$

**11.38** (a)  $1 + \frac{R_2}{R_1} = 11 \text{ V/V}$ ; (b)  $0.1 \text{ mA}, 0.3 \text{ mA}, +7.7 \text{ V}$ ; (c)  $A = \beta \frac{R_L \parallel (R_1 + R_2)}{R_s + r_{e1} + \frac{R_1 \parallel R_2}{\beta + 1}} =$

$$255.3 \text{ V/V}, R_i = R_s + r_{e1} + \frac{R_1 \parallel R_2}{\beta + 1} = 0.359 \text{ k}\Omega, R_o = R_L \parallel (R_1 + R_2) = 0.917 \text{ k}\Omega; \text{(d)}$$

$$\beta = \frac{R_1}{R_1 + R_2} = 1/11; \text{(e)} 10.55 \text{ V/V}, 8.59 \text{ k}\Omega, 39.4 \Omega, 4\% \text{ less}$$

**11.40** (b)  $0 \text{ V}, 0 \text{ V}$ ; (c)  $A = g_{m1,2} (r_{o2} \parallel r_{o4}) \parallel R_{22} = 47.62 \text{ V/V}$ ; (d)  $821 \text{ k}\Omega, 179 \text{ k}\Omega$ ; (e)  $5 \text{ k}\Omega$ ; (f)  $3.33 \text{ V/V}$ ; (g)  $3.33 \text{ V/V}$

**11.42** (b)  $80 \text{ k}\Omega$ ; (d)  $928.5 \text{ V/V}$ ; (e)  $0.2 \text{ V/V}, 186.7$ ; (f)  $4.97 \text{ V/V}$ ; (g)  $19.98 \text{ M}\Omega$ ; (h)  $2.66 \Omega$ ; (i)  $18.67 \text{ kHz}$ ; (j)  $-0.47\%$

**11.44**  $0.1 \text{ V/mA}; 9.9 \text{ mA/V}; 1.01 \text{ M}\Omega; 0.99 \Omega$

**11.45** (a)  $1/R_F$ ; (b)  $100 \Omega$ ; (c)  $\frac{\mu R_F}{\frac{1}{g_m} + R_F}$ ; (d)  $166.7, 1667 \text{ mA/V}; 9.94 \text{ mA/V}$

**11.48**  $4.87 \text{ mA/V}; 1.11 \text{ M}\Omega; 4.1 \text{ M}\Omega$

**11.49**  $100 \Omega; 497 \text{ V/V}; 9.94 \text{ mA/V}$

**11.52** (a)  $A_f|_{\text{ideal}} = \frac{1}{R_{S1}} + \frac{1}{R_{S2}} + \frac{R_F}{R_{S1}R_{S2}}, 800 \Omega$ ; (b)  $0.01 \text{ V/mA}, 90 \Omega, 90 \Omega$ ; (c)  $5951 \text{ mA/V}$ ; (d)  $60.51, 98.3 \text{ mA/V}, 1.7\% \text{ lower, increase } R_F$ ; (e)  $29.1 \text{ k}\Omega, 1.76 \text{ M}\Omega$

**11.53** (a)  $800 \Omega$ ; (b)  $0.01 \text{ V/mA}$ ; (c)  $90 \Omega, 90 \Omega$ ; (d)  $1.687 \mu \text{ mA/V}$ ; (e)  $5868 \text{ V/V}$ ; (f)  $99 \text{ mA/V}$ ; (g)  $10 \text{ M}\Omega, 2.37 \text{ M}\Omega$

**11.58** (a)  $0 \text{ V}, +0.6 \text{ V}, +0.6 \text{ V}$ ; (b)  $1/R_F, 0.1 \text{ mA/V}$ ; (c)  $0.099 \text{ mA/V}$ ; (d)  $202 \text{ M}\Omega$ ; (e)  $0.99 \text{ V/V}, 1.26 \Omega$

**11.60**  $0.94 \text{ V/mA}; 28.3 \Omega; 21.1 \Omega$

**11.62** (a)  $-R_F/R_s, 100 \text{ k}\Omega$ ; (b)  $-9.89 \text{ V/V}, 100.9 \Omega, 11 \Omega$ ; (c)  $180.2 \text{ kHz}$

**11.65** (a)  $+0.5 \text{ V}, +1.0 \text{ V}, +0.5 \text{ V}$ ; (b)  $4 \text{ mA/V}, 20 \text{ k}\Omega$ ; (c)  $A = -g_{m1} r_{o1} R_F \frac{R_F \parallel r_{o2}}{(R_F \parallel r_{o2}) + 1/g_{m2}}$ ;

$$(d) -1/R_F; g_{m1} r_{o1} \frac{R_F \parallel r_{o2}}{(R_F \parallel r_{o2}) + 1/g_{m2}}; (e) -\frac{g_{m1} r_{o1} R_F (R_F \parallel r_{o2})}{(R_F \parallel r_{o2}) + 1/g_{m2} + (g_{m1} r_{o1})(R_F \parallel r_{o2})};$$

$$(f) R_F, R_F \left[ 1 + g_{m1} r_{o1} \frac{R_F \parallel r_{o2}}{(R_F \parallel r_{o2}) + 1/g_{m2}} \right], \left( R_F \parallel r_{o2} \parallel \frac{1}{g_{m2}} \right), \left( R_F \parallel r_{o2} \parallel \frac{1}{g_{m2}} \right) /$$

$$\left[ 1 + g_{m1} r_{o1} \frac{R_F \parallel r_{o2}}{(R_F \parallel r_{o2}) + 1/g_{m2}} \right]; (g) -1561 \text{ k}\Omega, -0.05 \text{ mA/V}, 78 - 19.8 \text{ k}\Omega, 20 \text{ k}\Omega,$$

$$244 \Omega, 253 \Omega, 3.1 \Omega$$

- 11.67** (a) +0.75 V; (b) -456 k $\Omega$ , 3.33 k $\Omega$ , 119  $\Omega$ ; (c) -0.1 mA/V, 45.6, 46.6; (d) -9.79 k $\Omega$ , 71.5  $\Omega$ , 2.6  $\Omega$
- 11.68** 20 k $\Omega$ ; -19 k $\Omega$ ; 24;  $\Omega$ ; 488  $\Omega$
- 11.70** (a) 100  $\mu$ A, 60 k $\Omega$ , 30 k $\Omega$ , 12.5 12.5, (b)  $-R_2/R_s$ ,  $-1/R_2$ ; (c) 6 k $\Omega$ ; (d) -404 k $\Omega$ , 4.62 k $\Omega$ , 875  $\Omega$ ; (e) -4.65 V/V; (f) 337  $\Omega$ , 61  $\Omega$
- 11.72** 10 k $\Omega$ ; 990 k $\Omega$ ; -1020 V/V; 1.02 G $\Omega$
- 11.74** (a) +0.7 V; (b) -5 A/A, -0.2 A/A; (c) 2 mA/V, 50 k $\Omega$ ; (d) 17.5 k $\Omega$ , -525.8 A/A, 332.8 k $\Omega$ ; (e) 105.16, -4.95 A/A; (f) 164.8  $\Omega$ , 35.3 M $\Omega$
- 11.80** (a) 0.865 mA, 0.77 mA; (c) 3.94 A/A, 3.47 A/A; (d) -0.254 A/A; (e) -216.3 A/A, 1.68 k $\Omega$ , 2.67 k $\Omega$ ; (e) 54.9, 55.9, -3.87 A/A, 30.1  $\Omega$ , 149.2 k $\Omega$ ; (g) 30.2  $\Omega$ , -3.41 A/A, 9.17 M $\Omega$
- 11.81**  $10^4$  rad/s; 0.02; 50
- 11.83**  $1.095 \times 10^5$  rad/s;  $2.42 \times 10^{-3}$
- 11.84**  $10^4$  V/V; 1 MHz; 10 MHz;  $(1 + A_0\beta)$
- 11.87** 0.049; 980 kHz; 700 kHz
- 11.89** 2; 173.2 kHz
- 11.91**  $3.085 \times 10^3$  Hz;  $18.15^\circ$ ;  $10^{-3}$ ; 60 dB
- 11.93** 87.6 dB; 81.8 dB
- 11.96** 200 Hz
- 11.98** (a) 10 kHz; 100 Hz

## Chapter 12

- 12.2**  $-1.1 \text{ V} < v_o < 1.91 \text{ V}$ ;  $-1.6 \text{ V} < v_i < 3 \text{ V}$
- 12.4**  $R = 152\Omega$ ;  $A_v = 0.998, 0.996, 0.978$  V/V; 2%
- 12.7**  $V_{cc}I$
- 12.9**  $\hat{V}$ ;  $\hat{V}/R_L$ ; 25%
- 12.10** 2.5 V
- 12.12** 4.5 V; 6.4%; 625  $\Omega$
- 12.14** 10 V; 6.37 V; 2.74  $\Omega$ , 18.25 W; 3.86  $\Omega$ , 3.24 W
- 12.18** 1.382 V; 12.5  $\Omega$ ; 0.889 V/V; 0.998 V/V
- 12.20** 4.9 mA
- 12.23** 1.35 mA; -1.05 V; +4 V; -6 V
- 12.25** 1.96 mA;  $-10 \text{ V} < v_o < 5.1 \text{ V}$ ; 99; 3.92 mA; 3.84 mA
- 12.27**  $-g_{m3}\beta R_L$
- 12.30** 1.34 k $\Omega$ ; 1.04 k $\Omega$
- 12.32** 60.2  $\Omega$
- 12.36** (a) 9.1 mA; 0 mA; 0 V; (b) 220  $\Omega$ ; 0.93 V/V; 1.51  $\Omega$
- 12.38** (a) 0.0144 mA; 1.44 mA; (b) -43.6 V/V; (c) 137.1 k $\Omega$
- 12.41** (a) 30.5 V; (b)  $246.8/R_L$ ;  $881.8/R_L$
- 12.43** 4.3  $\Omega$ ; 325 mV; 4.4 nA

**12.45** 35 mA; 5 mA**12.47** 10  $\Omega$ **12.50** (a) 533.3; 1333.3; (b) 10 V/V; (c) 5%; (d)  $\pm 1.85$  V; (e) +0.3 V; -0.3 V; (f)  $-1.77 \text{ V} \leq v_o \leq +1.77 \text{ V}$ **12.52** +4 V; -4 V**12.54** 2 W; +5 V; 3 W; +5 V; 600 mA; 30 V

## Chapter 13

**13.1**  $-0.8 \text{ V} \leq V_{ICM} \leq +0.2 \text{ V}; -0.8 \text{ V} \leq v_o \leq +0.8 \text{ V}$ **13.3** 0.15 V**13.6** 0.8 pF; 477.5 MHz; 477 MHz**13.8** 3.18 pF; 0.1 mA; 0.3 mA**13.10** 3.2 pF; 30 MHz**13.12** 62.8 V/ $\mu$ s; 1.6 pF**13.14** 11.4 MHz**13.16** 636 k $\Omega$ **13.18** 318.3 kHz; 8.0 MHz**13.20** (a) 1 pF; (b) 0.41 pF**13.23** (a) 0.16 V; (b) 2 pF; (c) 78.1**13.25** (b) 0.45  $\mu$ m**13.27** +0.3 V; +0.45 V; -0.45 V; -0.3 V  $\leq V_{ICM} \leq +1.25$  V; -0.3 V  $\leq v_o \leq +0.7$  V**13.29** 1 mA/V; 833 k $\Omega$ ; 833 V/V; 9.88 V/V; 10 k $\Omega$ **13.31**  $I/C_L$ **13.36** (a)  $-0.25 \text{ V} \leq V_{ICM} + 1.3 \text{ V}$ ; (b)  $-1.3 \text{ V} \leq V_{ICM} + 0.25 \text{ V}$ ; (c)  $-0.25 \text{ V} \leq V_{ICM} + 0.25 \text{ V}$ ; (d)  $-1.3 \text{ V} \leq V_{ICM} + 1.3 \text{ V}$ **13.38** 0.176 $C_L$ **13.40** 6.93 k $\Omega$ ; 40 k $\Omega$ ; 40 k $\Omega$ **13.43** 1.8 k $\Omega$ **13.45**  $A_7 = 3A_3; A_8 = 10A_3; R_3 = R_4 = 6.67 \text{ k}\Omega; R_7 = 2.22 \text{ k}\Omega; R_8 = 667\Omega$ **13.47** (a) 0.1 V  $\leq V_{ICM} \leq 2.2$  V; (b) 0.8 V  $\leq V_{ICM} \leq 2.9$  V**13.50** 125 k $\Omega$ ; 95.4 V/V**13.52** (b) 367.3; (c) 6.75 mV**13.56** 2**13.58**  $190 \leq \beta_N \leq 211$ **13.60** 105.3 dB**13.63** 50  $\mu$ A**13.65**  $R_1 = 5.76k\Omega; R_2 = 6.22k\Omega; 521 \Omega$ **13.67** (a)  $0.1 \text{ V} \leq v_o \leq 2.9 \text{ V}$ ; (b) 20 k $\Omega$ ; (c) 0.2  $\Omega$ ; (d) 12.3 mA; 0.3 mA; 1.6 k $\Omega$ ; (e) 12.3 mA; 0.3 mA; 2.4 k $\Omega$ **13.70** 10.6  $\mu$ A; minimum current is 0.3 mA

## Chapter 14

**14.2** (a) 0.995 V,  $-5.7^\circ$ ; (b) 0.707,  $-45^\circ$ , (c) 0.1 V,  $-84.3^\circ$ ; (d) 0.01 V,  $-89.4^\circ$

**14.4** 1 V/V; 0.944 V/V; 0.0001 V/V

**14.5** 0.59 dB; 60 dB; 1.2

**14.7** 0.509 rad/s; 3 rad/s; 5.89

**14.10** 3; low-pass;  $\frac{0.3125(s^2 + 4)}{(s+1)(s^2 + s + 1.25)}$

**14.12** 4;  $\frac{4.512 \times 10^5 s^2}{(s^2 + s \cdot 10^3 + 10^6)(s^2 + s \cdot 10^2 + 1.44 \times 10^6)}$

**14.13**  $\frac{0.17(s^2 + 6.25)}{s^2 + 0.5s + 1.0625}$ ; 0.17

**14.15**  $1/(s^3 + 2s^2 + 3s + 2)$ ; All zeros at  $s = \infty$ ; Poles:  $s = -1$ ,  $s = -0.5 \pm j1.323$

**14.18**  $10^9/(s^2 + s \cdot 1.414 \times 10^4 + 10^8)$

**14.21**  $\frac{0.64(s^2 + 1.5625 \times 10^8)}{s^2 + 5 \times 10^3 s + 10^8}$ ; 0.64

**14.26** (a) 1 rad/s,  $1/\sqrt{2}$ , 12.3 dB; (b) 0.8427 rad/s, 1.3, 17 dB

**14.28**  $\frac{s^2}{s^2 + s + 1}$ ; 1 rad/s; 1

**14.32** 42.1 dB

**14.34** 7; 23.15 dB, 0.25 dB

**14.36** 7; Poles:  $\omega_0 = 2\pi \times 10^4$  rad/s,  $Q_1 = 2.247$ ,  $Q_2 = 0.802$ ,  $Q_3 = 0.555$ , real pole at

$$s = -2\pi \times 10^4; \frac{\omega_0^7}{(s^2 + s \frac{\omega_0}{2.247} + \omega_0^2)(s^2 + s \frac{\omega_0}{0.802} + \omega_0^2)(s^2 + s \frac{\omega_0}{0.555} + \omega_0^2)(s + \omega_0)};$$

66.8 dB

**14.39** 45.3 dB

**14.40** Peaks:  $0.95 \omega_p$ ,  $0.59 \omega_p$ , 0; Valleys:  $\omega_p$ ,  $0.81 \omega_p$ ,  $0.31 \omega_p$

**14.42** (a) 10, 4 dB;

(b)  $p_{1,10} = \omega_p(-0.0224 \pm j0.9978)$ ,

$p_{2,9} = \omega_p(-0.0651 \pm j0.9001)$ ,

$p_{3,8} = \omega_p(-0.1013 \pm j0.7143)$ ,

$p_{4,7} = \omega_p(-0.1277 \pm j0.4586)$ ,

$p_{5,6} = \omega_p(-0.1415 \pm j0.1580)$ ;

$$\frac{7.60 \times 10^{40}}{(s^2 + s \cdot 0.0448 \omega_p + 0.9961 \omega_p^2)(s^2 + s \cdot 0.1302 \omega_p + 0.8144 \omega_p^2)} \times$$

$$\frac{1}{(s^2 + s \cdot 0.2026 \omega_p + 0.5205 \omega_p^2)(s^2 + s \cdot 0.2554 \omega_p + 0.2266 \omega_p^2)}$$

$$\frac{1}{(s^2 + s \cdot 0.2830 \omega_p + 0.0450 \omega_p^2)}$$

**14.44** 2 nF, 12.5 mH

- 14.46** (a)  $C_1/(C_1 + C_2)$ ,  $C_1/(C_1 + C_2)$ , no zeros; (b) 0,  $C_1/(C_1 + C_2)$ , zero at  $s = 0$ ; (c)  $L_2/(L_1 + L_2)$ ,  $L_2/(L_1 + L_2)$ , no zeros; (d) 0,  $L_2/(L_1 + L_2)$ , zero at  $s = 0$

$$\text{14.51 } V_o = \frac{s^2 V_y + s \left( \frac{\omega_0}{Q} \right) V_z + \omega_0^2 V_x}{s^2 + s \left( \frac{\omega_0}{Q} \right) + \omega_0^2}$$

- 14.52**  $R_1 = R_2 = R_3 = R_5 = 10 \text{ k}\Omega$ ; (a)  $C_4 = 0.1 \mu\text{F}$ ; (b)  $C_4 = 10 \text{ nF}$ ; (c)  $C_4 = 1 \text{ nF}$

- 14.56** First-order section:  $T_1(s) = \frac{2 \times 10^4}{s + 10^4}$ ,  $R_1 = 50 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $C = 1 \text{ nF}$ ;

Second-order section:  $T_2(s) = \frac{2 \times 10^8}{s^2 + s \frac{10^4}{1.618} + 10^8}$ ,  $C = 1 \text{ nF}$ ,  $R = 100 \text{ k}\Omega$ ,  $R_6 =$

$1.618 \text{ k}\Omega$ ,  $K = 2$ ; Second-order section:  $T_3(s) = \frac{2.5 \times 10^8}{s^2 + s \frac{10^4}{0.618} + 10^8}$ ,  $C = 1 \text{ nF}$ ,

$$R = 100 \text{ k}\Omega, R_6 = 61.8 \text{ k}\Omega, K = 2.5$$

- 14.59**  $R = 2 \text{ k}\Omega$ ,  $C = 796 \text{ pF}$ ,  $R_6 = 200 \text{ k}\Omega$

$$\text{14.60 (a) } T(s) = \frac{0.4508 \times 10^5 (s^2 + 1.6996 \times 10^{10})}{(s + 0.7294 \times 10^5)(s^2 + s 0.2786 \times 10^5 + 1.0504 \times 10^{10})}$$

- (b) First-order section:  $R_1 = R_2 = 13.71 \text{ k}\Omega$ ,  $C = 1 \text{ nF}$ , Second-order section:  $R_1 = R_2 = R_3 = R_5 = 9.76 \text{ k}\Omega$ ,  $C_{61} = 618 \text{ pF}$ ,  $C_{62} = 382 \text{ pF}$ ,  $R_6 = 35.9 \text{ k}\Omega$ ,  $K = 1$

- 14.61**  $C = 10 \text{ nF}$ ,  $R = 5.31 \text{ k}\Omega$ ,  $R_1 = 10 \text{ k}\Omega$ ,  $R_f = 10 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ ,  $R_3 = 119 \text{ k}\Omega$ ,  $K = 1.983$ , gain = 119 V/V

$$\text{14.64 } R = 1/\omega_0 C; R_1 = \infty, C_1 = GC, R_2 = \left( \frac{R}{G} \right) \left( \frac{\omega_0}{\omega_n} \right)^2, R_3 = \infty$$

- 14.68**  $C_1 = C_2 = 10 \text{ nF}$ ,  $R_3 = 12.73 \text{ k}\Omega$ ,  $R_4 = 200 \Omega$ , gain = -32 V/V

- 14.72** Second-order section:  $R_1 = R_2 = 10 \text{ k}\Omega$ ,  $C_3 = 492 \text{ pF}$ ,  $C_4 = 5.15 \text{ nF}$ ; Second order section:  $R_1 = R_2 = 10 \text{ k}\Omega$ ,  $C_3 = 1.29 \text{ nF}$ ,  $C_4 = 1.97 \text{ nF}$ ; First-order section:  $R_1 = R_2 = 10 \text{ k}\Omega$ ,  $C = 1.59 \text{ nF}$

- 14.73** 100 MΩ; 20 MΩ; 10 MΩ; 2 MΩ; 1 MΩ

- 14.77** 0.1 pF; 0.1 pF; 0.1414 pF; 0.1 pF

## Chapter 15

- 15.1**  $\omega_0$ ; 1/A

- 15.3** (a) 100 pF; (b) 50 kΩ; (c) 0.001

- 15.5** 0.6 mA/V; 15.92 MHz

$$\text{15.8 } s^2 + s \frac{1}{CR} \left( 2 - \frac{r_2}{r_1} \right) + \frac{1}{C^2 R^2}; 2; 1/CR$$

- 15.10** 2.55 V

- 15.11** 0.125%; 0.042%
- 15.14**  $0.878/CR$
- 15.16**  $6.6 \text{ k}\Omega$ ,  $6.6 \text{ k}\Omega$ ;  $\hat{V}_0 = 1.05 \text{ V}$
- 15.19** 7.88 V
- 15.20**  $C = 1.59 \text{ nF}$ ; 8.6 kHz; change the shunt resistor to  $7.5 \text{ k}\Omega$  and  $R_2/R_1$  to 2.35.
- 15.26**  $C = 1.59 \text{ nF}$ ;  $R_f$  slightly smaller than  $20 \text{ k}\Omega$ ;  $R_3 = 2.74 \text{ k}\Omega$ ;  $R_4 = 10 \text{ k}\Omega$
- 15.28**  $4.97 \text{ k}\Omega$ ; 3.6 V; add a diode in series with each of the diodes in the limiter.
- 15.29** (a) 0; (b)  $4.17 \times 10^{-3}$ ; (c)  $1.39 \times 10^{-3}$ ; (d)  $4.5 \times 10^{-3}$  or 0.45%
- 15.30**  $j\omega[-\omega^2 LC_1 C_2 + (C_1 + C_2)] + \left(g_m + \frac{1}{R_L} - \omega^2 \frac{LC_2}{R_L}\right) = 0$ ;  

$$\omega_0 = 1/\sqrt{L\left(\frac{C_1 C_2}{C_1 + C_2}\right)}; g_m R_L = \frac{C_2}{C_1}$$
- 15.33**  $L_1 = 2.41 \mu\text{H}$ ;  $L_2 = 0.12 \mu\text{H}$
- 15.35**  $C = 1.25 \text{ pF}$ ;  $g_m = 2.7 \text{ mA/V}$
- 15.36** 2.0165 MHz to 2.0173 MHz, an 800 Hz range.
- 15.37** 30 kΩ
- 15.43** (a) either +5 V or -5 V; (b) symmetric square wave of frequency  $f$ , lagging the sine wave by  $65.4^\circ$ , having  $\pm 5 \text{ V}$  swing; 0.1 V
- 15.44** 9.518 kHz

## Chapter 16

- 16.1** (a)  $1.90 \text{ k}\Omega$  (b)  $10.26 \text{ k}\Omega$  (c) 8.1
- 16.2** (a) 6.0 (b)  $1.67 \text{ k}\Omega$
- 16.16**  $NM_H = 0.5 \text{ V}$ ;  $NM_L = 0.4 \text{ V}$
- 16.18**  $NM_H = 0.2V_{DD}$ ;  $NM_L = 0.3V_{DD}$ ; transition region width = 0.2  $V_{DD}$ ;  $V_{DD} = 1.25 \text{ V}$
- 16.20**  $V_M = V_{IL} = V_{IH} = 0.9 \text{ V}$ ;  $V_{OL} = 0 \text{ V}$ ;  $V_{OH} = 1.8 \text{ V}$ ;  $NM_L = NM_H = 0.9 \text{ V}$ ; gain =  $\infty$
- 16.23**  $V_{DD} = 1.0 \text{ V}$ ;  $R_D = 31.6 \text{ k}\Omega$ ;  $W/L = 1.7$ ;  $P_D$  (high output) =  $30 \mu\text{W}$ ;  $P_D$  (low output) = 0
- 16.24**  $V_{DD} = 1.2 \text{ V}$ ;  $R_D = 27.6 \text{ k}\Omega$ ;  $W/L = 2.1$ ;  $V_{IL} = 0.435 \text{ V}$ ;  $V_M = 0.6 \text{ V}$ ;  $V_{IH} = 0.7 \text{ V}$ ;  $NM_L = 0.385 \text{ V}$ ;  $NM_H = 0.5 \text{ V}$
- 16.28** (a)  $W_p = 527 \text{ nm}$ ; area =  $40,560 \text{ nm}^2$  (b)  $V_{OH} = 1 \text{ V}$ ;  $V_{OL} = 0 \text{ V}$ ;  $V_{IH} = 0.5375 \text{ V}$ ;  $V_{IL} = 0.4625 \text{ V}$ ;  $NM_H = NM_L = 0.4625 \text{ V}$  (c)  $r_{DSP} = r_{DSN} = 1.9 \text{ k}\Omega$
- 16.31** 3.5 mV; 15.4 mV
- 16.32** 135
- 16.35** (a) 84 nm (b)  $V_{OH} = 0.9 \text{ V}$ ;  $V_{OL} = 0 \text{ V}$ ;  $V_{IH} = 0.49 \text{ V}$ ;  $V_{IL} = NM_H = NM_L = 0.41 \text{ V}$  (c)  $r_{DSP} = r_{DSN} = 1.11 \text{ k}\Omega$  (d)  $r = 0.816$ ;  $V_M = 0.43 \text{ V}$

## Chapter 17

- 17.4**  $t_{PLH} = 27.6 \text{ ps}$ ;  $t_{PHL} = 13.8 \text{ ps}$ ;  $t_p = 20.7 \text{ ps}$
- 17.5** (a)  $V_{OL} = 0 \text{ V}$ ;  $V_{OH} = 1.2 \text{ V}$ ;  $NM_L = NM_H = 0.6 \text{ V}$  (b)  $t_{PHL} = 138 \text{ ps}$ ;  $t_{THL} = 440 \text{ ps}$   
 (c)  $t_{PLH} = 138 \text{ ps}$ ;  $t_{TLH} = 440 \text{ ps}$
- 17.7** (a) 475 ps (b) 400 ps;  $t_p = 175 \text{ ps}$
- 17.9**  $(W/L)_n \geq 1.95$ ;  $(W/L)_p \geq 7.8$
- 17.11** 293.3 ps
- 17.14**  $t_{PHL} = 34.4 \text{ ps}$ ;  $t_{PLH} = 42.6 \text{ ps}$ ;  $t_p = 38.5 \text{ ps}$ ;  $f_{max} = 13 \text{ GHz}$
- 17.16**  $t_{PHL} = t_{PLH} = t_p = 7.7 \text{ ps}$ ; 3.16 fF
- 17.17**  $S = 3$ ; area increases by a factor of 3
- 17.23** (a) 0.54 V (b) 0.47 V
- 17.24** (a)  $x = 6.32$ ;  $t_p = 25.3 \text{ CR}$  (b)  $n = 7$ ;  $x = 2.87$ ;  $t_p = 20.1 \text{ CR}$
- 17.26** 4.32 fJ; 54 W; 45 A
- 17.28** 0.175 pF
- 17.30** 0.188 pJ
- 17.35** (a) 0.184 to 0.216 mA (b) 46.3 to 54.3 ps

## Chapter 18

- 18.2** 0.834 V
- 18.4** 25.8 ps
- 18.6**  $V_{OH} = 0.59 \text{ V}$ ;  $V_{OL} = 0 \text{ V}$ ;  $i_{DP}(V_{OH}) = 1.08 \mu\text{A}$ ;  $t_{PLH} = 51.6 \text{ ps}$ ;  $t_{PHL} = 27.0 \text{ ps}$
- 18.7** (a)  $V_{DD}$  (b)  $|V_m|$  (c) 178 ps
- 18.11** 64.3 ps
- 18.18**  $V_M = 0.46 \text{ V}$ ;  $(W/L)_{5-8} = 1.42$
- 18.23** 4.5
- 18.24** (a) (1.64,0.385) (b) (3,0.5) (c) (3.69,0.538)
- 18.26**  $(W/L)_5/(W/L)_1 \leq 0.397$ ;  $W_5 = 65 \text{ nm}$ ;  $W_1 = 164 \text{ nm}$
- 18.29** (a) 3 (b) 4.93 ns (c) 3.33 ns
- 18.31**  $(W/L)_p \leq 3(W/L)_a$
- 18.34** 1024 cells; 10 address rows; 12 bits
- 18.38** 222 ps; 200 MHz
- 18.43** 10 address bits; 1024 output lines; 20 input lines; 11,264 transistors
- 18.45** 10 address bits; 10 levels of pass gates; 2046 transistors